

Postulates/Theorems of Boolean Algebra

P2	$x+0=x$	$x \cdot 1=x$
P3	$x+y=y+x$	$xy=yx$
P4	$x(y+z)=xy+xz$	$x+(y \cdot z)=(x+y)(x+z)$
P5	$x+\bar{x}=1$	$x \cdot \bar{x}=0$
T1	$x+x=x$	$x \cdot x=x$
T2	$x+1=1$	$x \cdot 0=0$
T3	$\overline{\overline{x}}=x$	
T4	$x+(y+z)=(x+y)+z$	$x \cdot (y \cdot z)=(x \cdot y) \cdot z$
T5	$\overline{(x+y)}=\bar{x} \cdot \bar{y}$	$\bar{x} \cdot \bar{y}=\overline{x+y}$
T6	$x+xy=x$	$x(x+y)=x$

We can now manipulate and/or simplify eqns.

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$f = m_3 + m_5 + m_6 + m_7$$

$$= \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

"cost" \Rightarrow 4 AND gates

1 OR gate

* inverter at input is free.

12 AND INPUTS

4 OR INPUTS

21

min term

$$f = \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$$

$$= \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz + xyz + xyz$$

$$= (\bar{x}+x)yz + x(\bar{y}+y)z + xy(\bar{z}+z)$$

$$= 1 \cdot yz + x \cdot 1 \cdot z + xy \cdot 1$$

$$= yz + xz + xy$$

product term

"cost" \Rightarrow 3 AND

1 OR

6 AND inputs

3 OR inputs

13



This is called a sum of products (SOP) impl. of f.

$$f = M_0 M_2 M_3 M_5 M_6$$

$$= (\underbrace{x+y+z}_{\text{max term}})(x+\bar{y}+z)(\bar{x}+\bar{y}+z)(\bar{x}+y+\bar{z})(\bar{z}+\bar{y}+z) \leftarrow \text{Canonical POS,}$$

$$= (\underbrace{x+z}_{\text{sum term}})(\bar{y}+z)(x+\bar{y})(\bar{x}+y+\bar{z}) \leftarrow \text{still a POS}$$

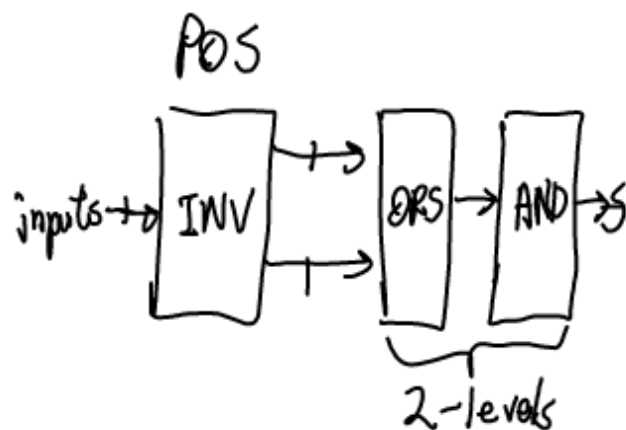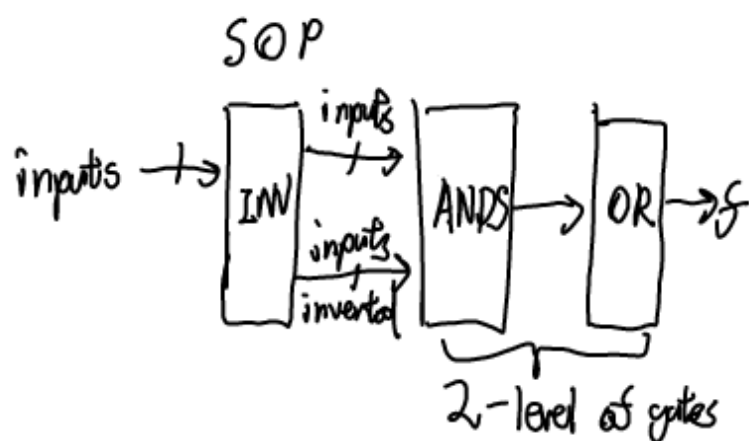POS + SOP are called "2-level" function implementations.




Other Logic Gates

XOR


2-inputs

x	y	$f = x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

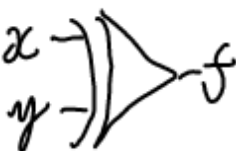


n-inputs "Odd"

x	y	z	$f = x \oplus y \oplus z$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

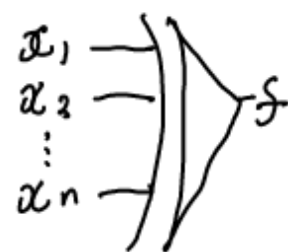


NXOR

x	y	$f = \overline{x \oplus y}$
0	0	1
0	1	0
1	0	0
1	1	1

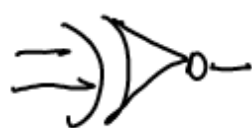


"Even"

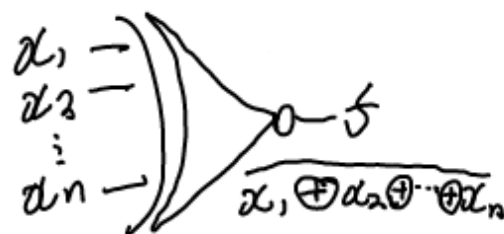


NOR "not or"

x	y	$f = \overline{x+y}$
0	0	1
0	1	0
1	0	0
1	1	0

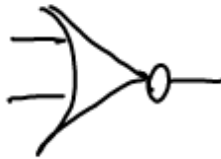

NAND "not and"

x	y	$f = \overline{xy}$
0	0	1
0	1	1
1	0	1
1	1	0




buffer

$x \rightarrow f$

x	f
0	0
1	1

tri-state buffer

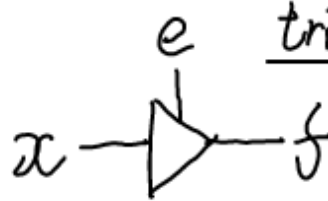

x	e	f
0	1	0
1	1	1
0	0	"Z"
1	0	"Z"

if $e=0$
 $x \rightarrow 0 \rightarrow f$
 disconnected

} buffer

"Z"