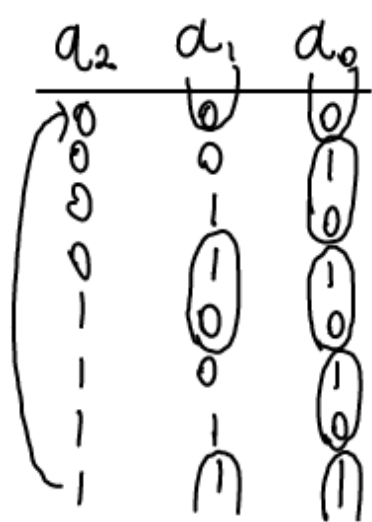





Last Time:



a_0 always flips

a_1 flips when a_0 goes $1 \rightarrow 0$

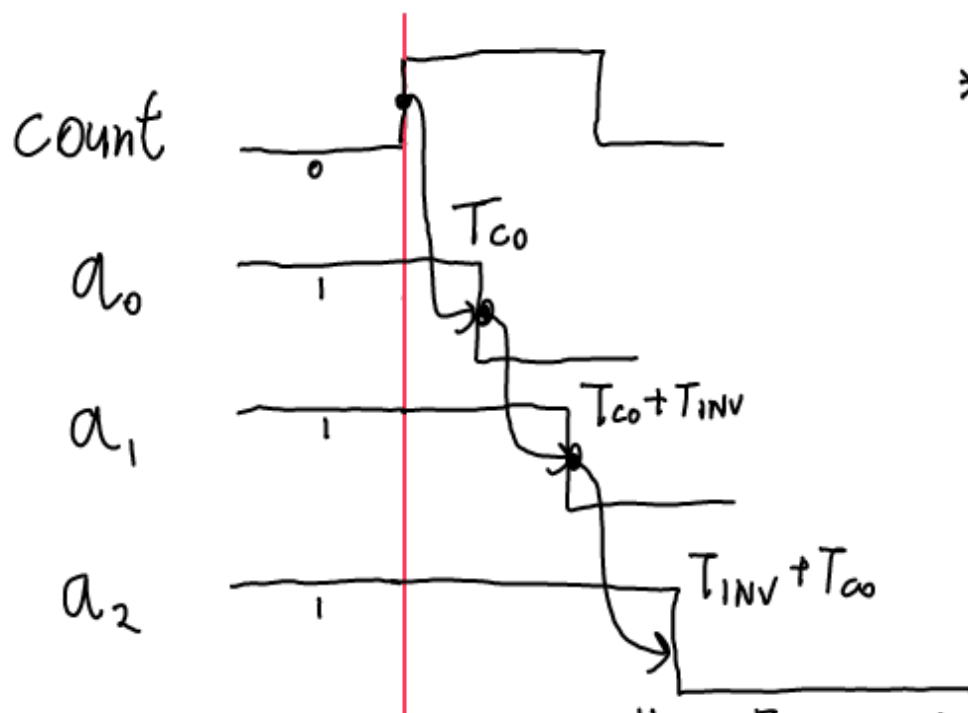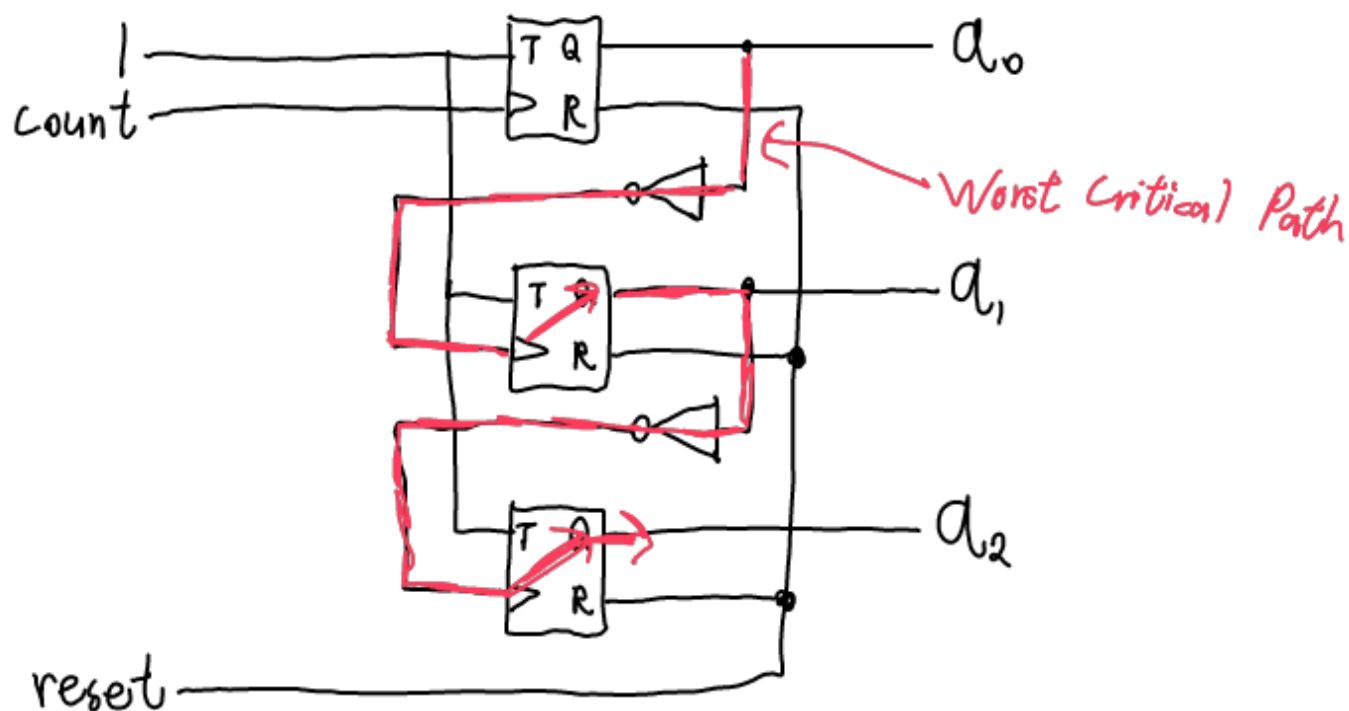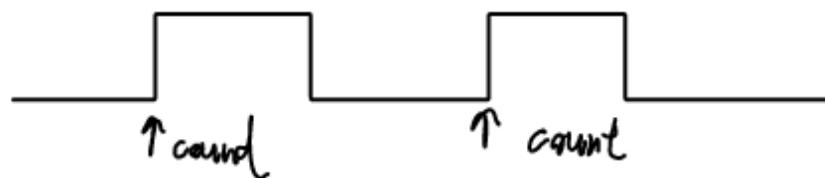a_2 flips when a_1 goes $1 \rightarrow 0$



* Ripple Counter

\Rightarrow Very Slow for large counters.

\Rightarrow Called asynchronous since each FF has a different clock.

* Can we make all FF update at the same time?


Synchronous Binary Counter - Same clock for all FFs.

a_2	a_1	a_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

a_0 always flips

a_1 flips when $a_0 = 1$

a_2 flips when $a_1 a_0 = 1$

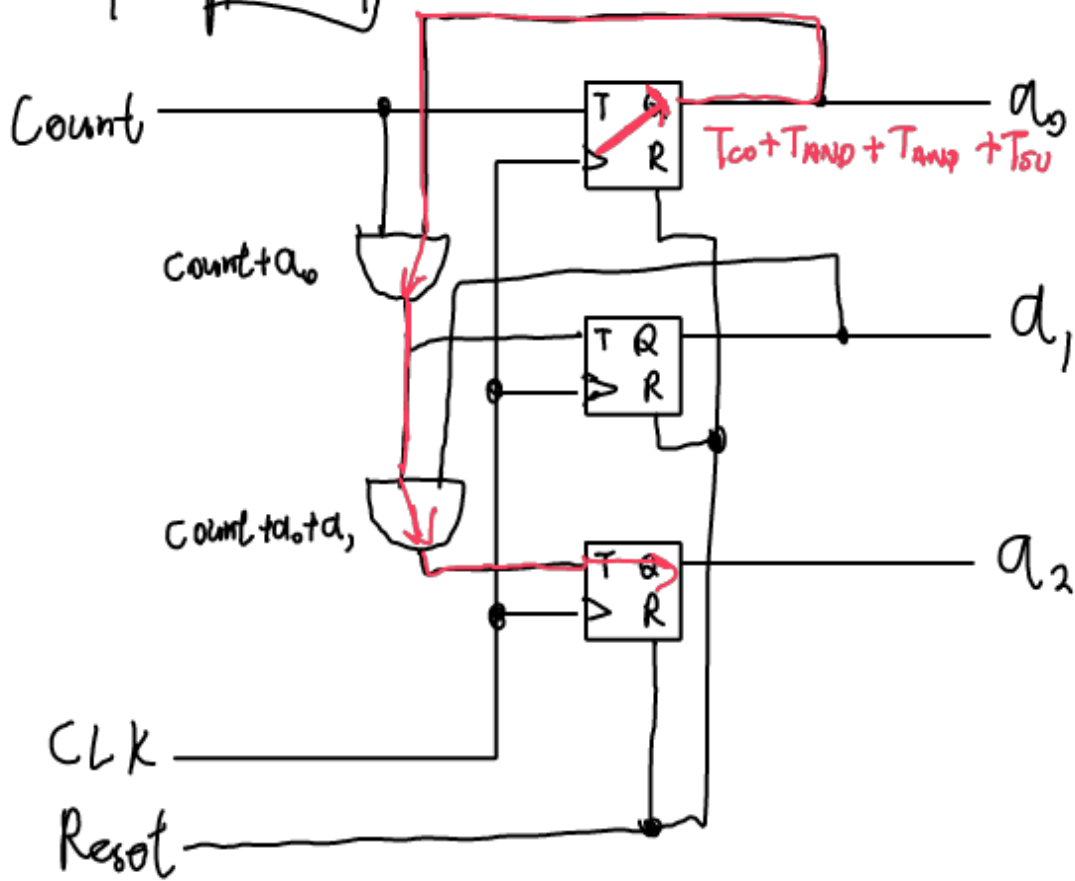


Down Counter

a_2	a_1	a_0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

a_0 always toggle

a_1 toggles when $a_0 = 0$



a_2 toggles when $a_1 a_0 = 00$

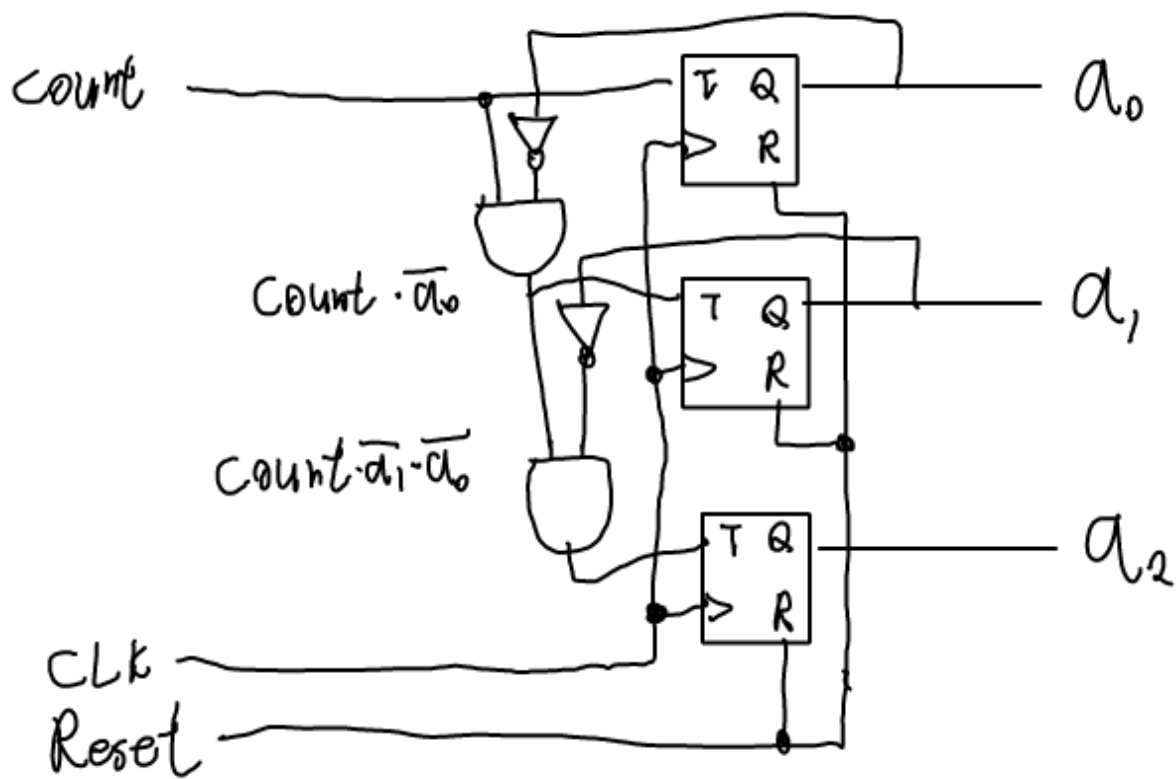

Let's make a circuit that can count up, count down, or hold.

up	down
0	0
0	1
1	X

hold
down
up

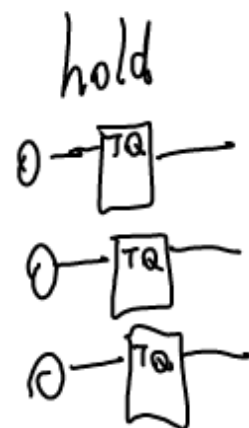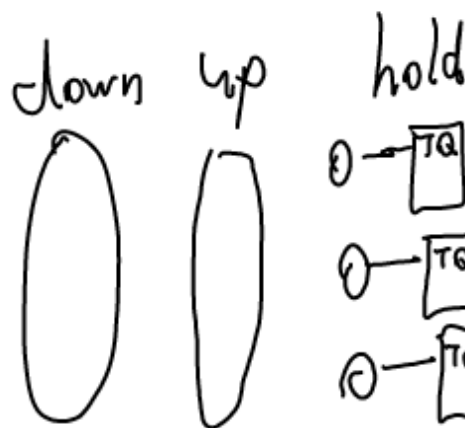

circuit on website