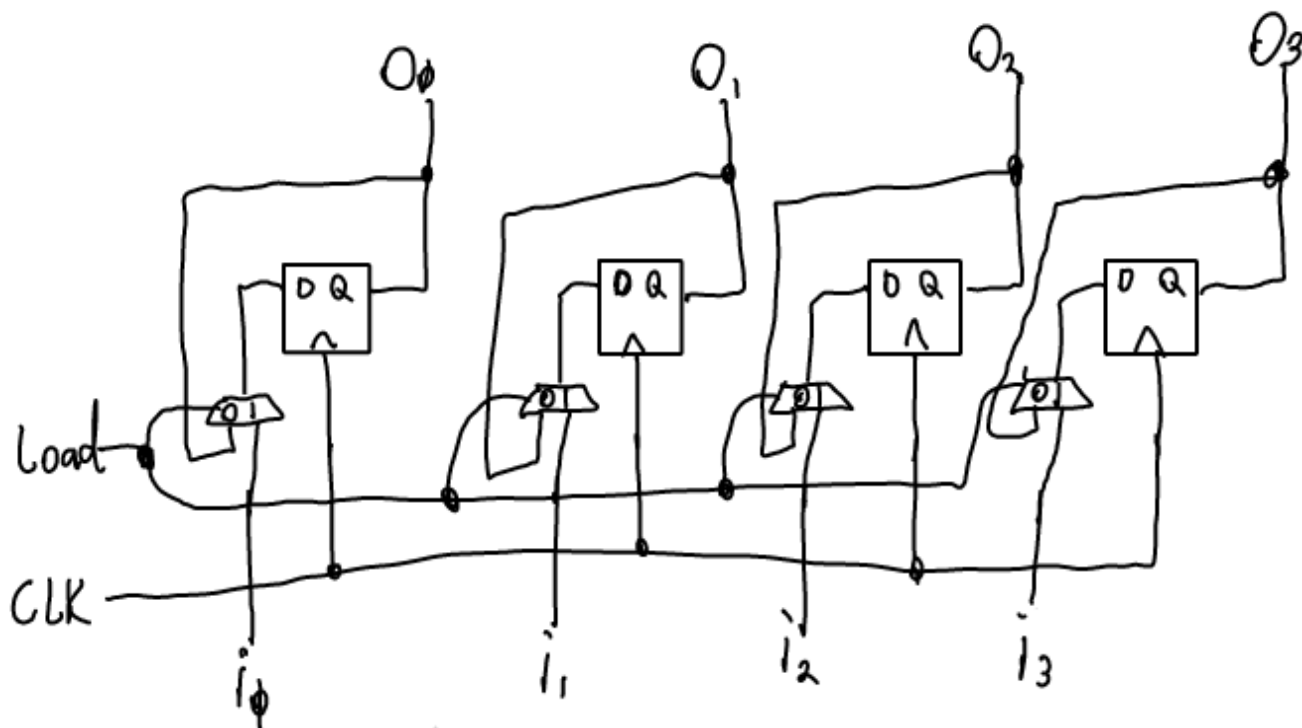


## Registers


Simply a bunch of flipflops "grouped together" to perform some function in which the bits are related. FFs typically clocked by the same clock.

e.g., design a 4-bit register that can either hold its current outputs or load some new data.


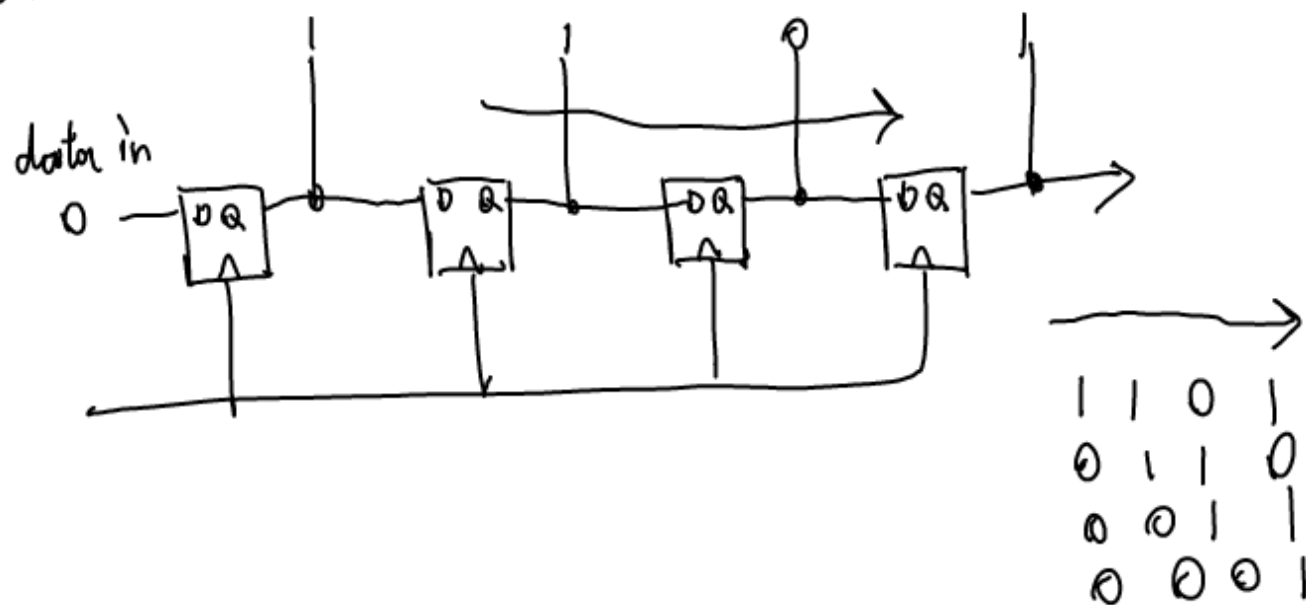
## Shift Registers

Connect outputs of register bits to make it look like data moves left-to-right (or right-to-left) as clock arrives.




# Universal Shift Registers

make a circuit that

- 1) can hold data;
- 2) can load new data in parallel;
- 3) can shift left;
- 4) can shift right.

$\Rightarrow$  do it for 3 bits.

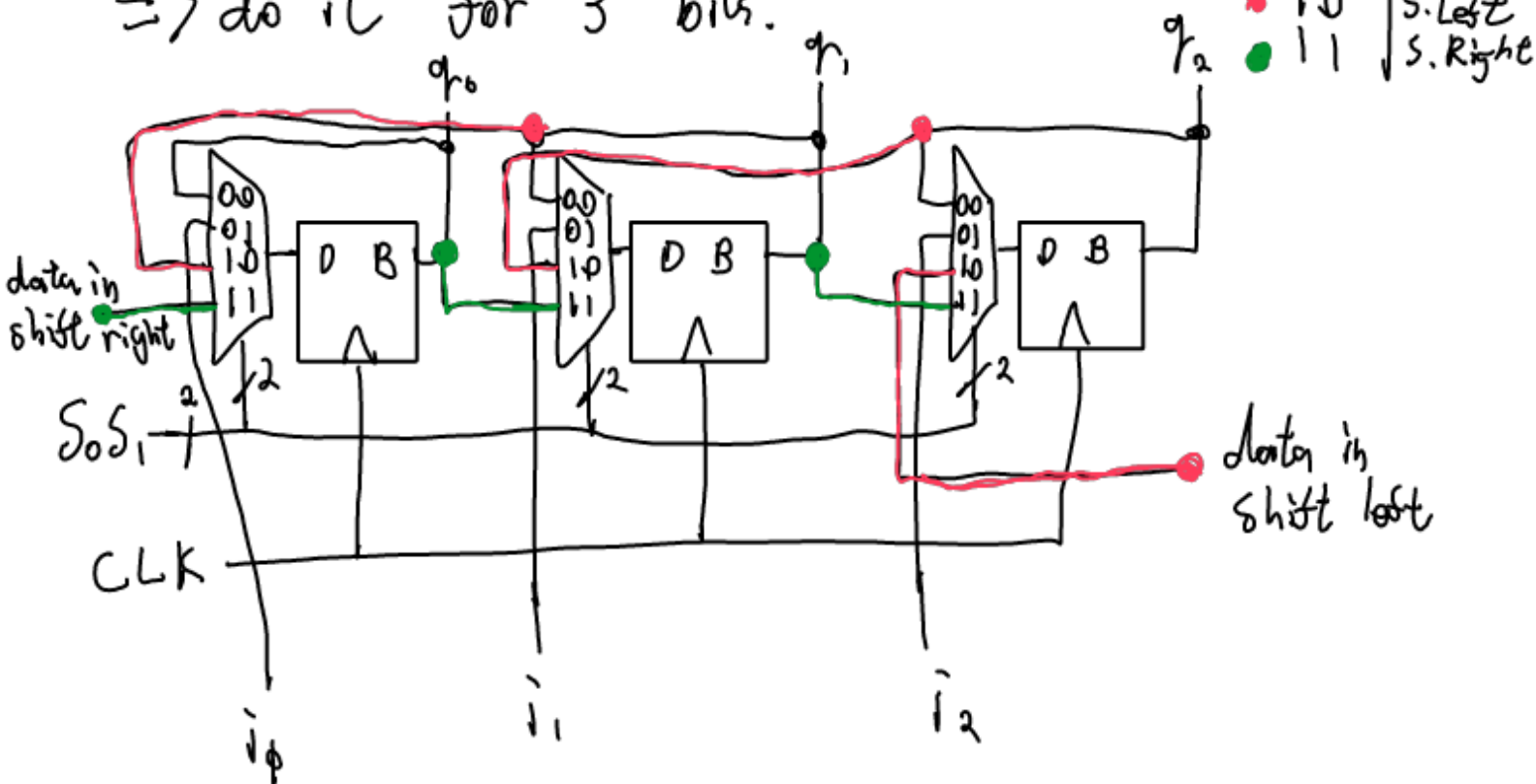

## Counters

\* A register whose output goes thru a prescribed sequence + repeats.

e.g., ①  $\rightarrow$  ②  $\rightarrow$  ③  $\rightarrow$  ④  $\rightarrow$  ①

000  
001  
111  
011

\* start with simple binary up-down counters.

n-flip-flops count  $0 \rightarrow 2^{n-1}$ , repeat (up)

$2^{n-1} \rightarrow 0$ , repeat (down)

# 4-bit counter

| $a_3$ | $a_2$ | $a_1$ | $a_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 0     |
| 0     | 0     | 1     | 1     |
| 0     | 1     | 0     | 0     |
| 0     | 1     | 0     | 1     |
| 0     | 1     | 1     | 0     |
| 0     | 1     | 1     | 1     |
| 1     | 0     | 0     | 0     |
| 1     | 0     | 0     | 1     |
| 1     | 0     | 1     | 0     |
| 1     | 0     | 1     | 1     |
| 1     | 1     | 0     | 0     |
| 1     | 1     | 0     | 1     |
| 1     | 1     | 1     | 0     |
| 1     | 1     | 1     | 1     |

$a_0$  always toggles

$a_1$  always toggles when  $a_0$  changes  $1 \rightarrow 0$

$a_2$  " " " "  $a_1$  "  $1 \rightarrow 0$