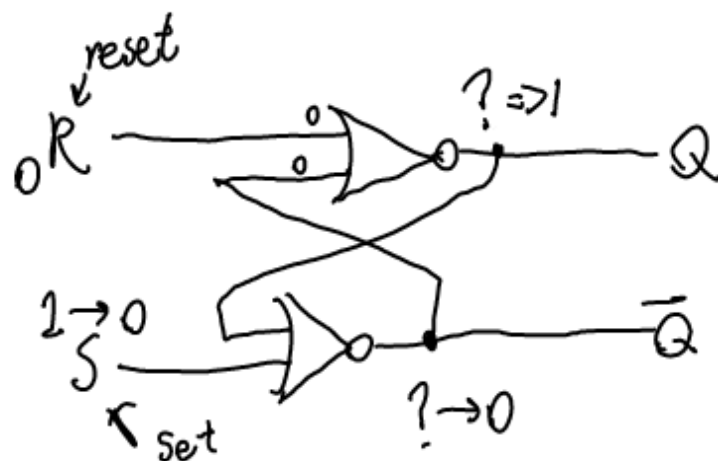


Latches - one type of memory element.

SR-Latch

0	0	1
0	1	0
1	0	0
1	1	0




How does this work + how does it have "memory"

S	R	Q	\bar{Q}	
1	0	1	0	← "set"
0	0	1	0	← "hold" (after SR=10)
0	1	0	1	← "reset"
0	0	0	1	← "hold" (after SR=01)
1	1	0	0	← "undesirable"

* Can set $Q=1$, can reset $Q=0$, can hold previous value.

$\overline{S}\overline{R}$ - Latch

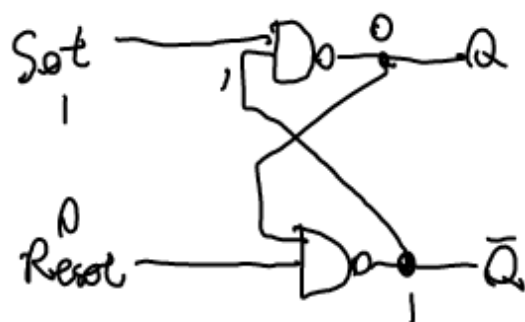


0	0	1
0	1	1
1	0	1
1	1	0

S	R	Q	\bar{Q}	
1	0	0	1	reset
1	1	0	1	hold
0	1	1	0	set
0	0	1	0	hold
0	0	1	1	← Undesirable


Gated Latch

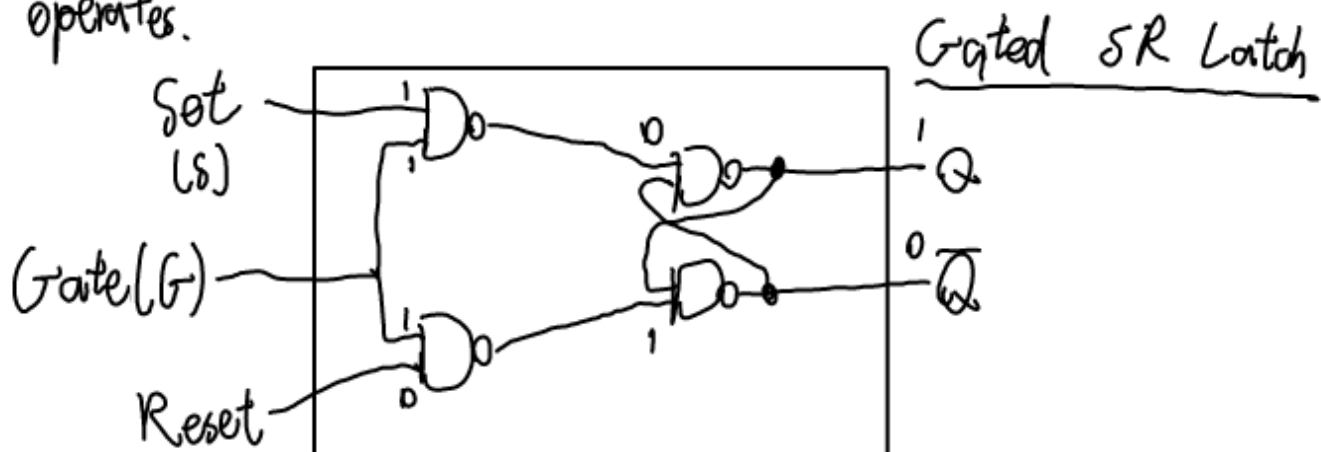* Add a "gate" to control whether or not the Latch operates.



Gate	Set	Reset	Q	\bar{Q}	
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Previous value		hold
1	1	1	1	1	Undesirable
0	X	X	Previous		hold

D-Latch

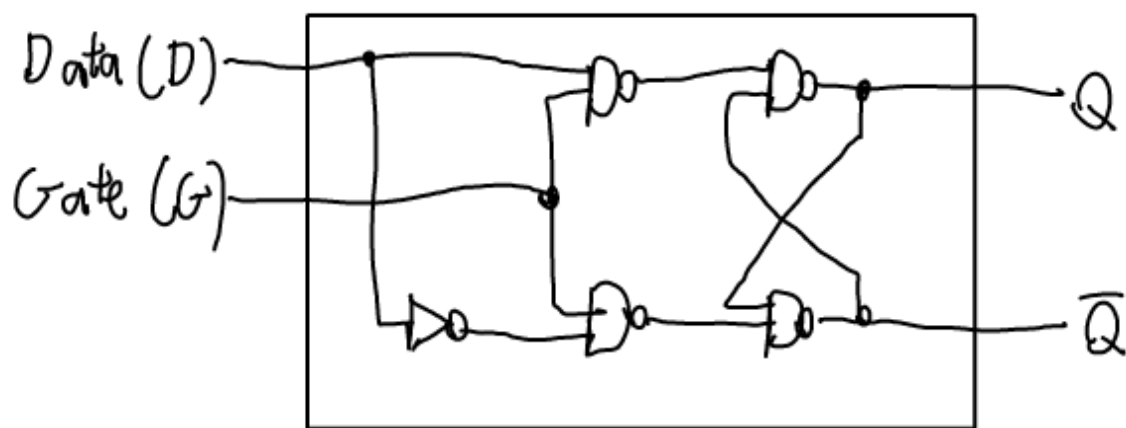


Gate	Data	Q	\bar{Q}	
1	1	1	0	set
1	0	0	1	reset
0	X	prev. val.		hold

* First set data
wait a bit — (let values become stable)
change the gate *



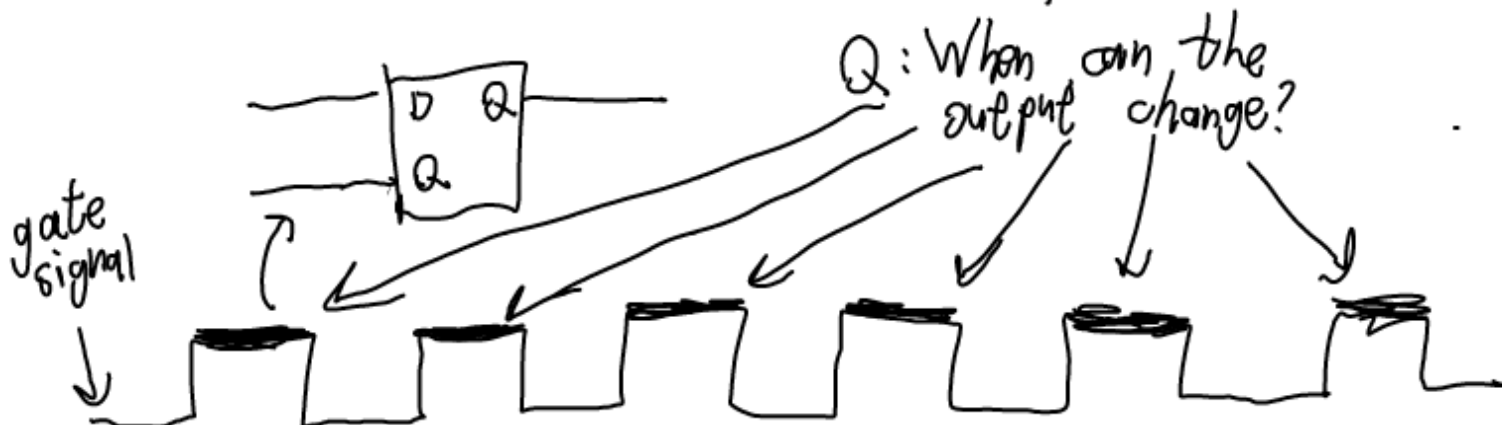
Latches are "level sensitive" memory elements.



- * Output changes whenever $G=1$ (i.e., on the "level of G ").
- * Would like a bit more control as to when Q can change.
- * The "interval" should be an "instant".

Flip Flops


Master-Slave Flip Flop

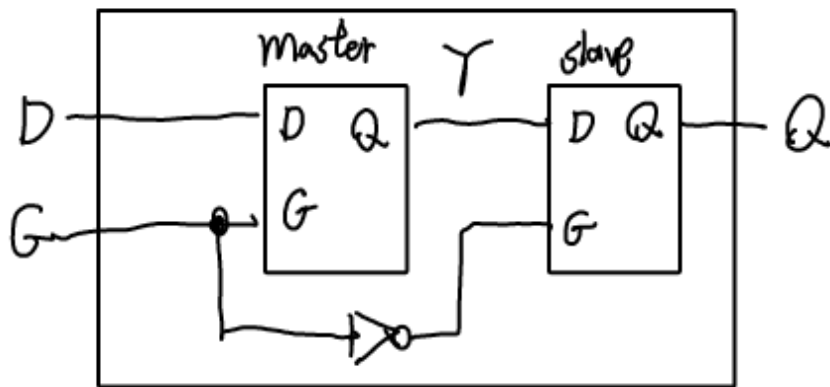

When $G=1$
 $Y=D$ (Y follows D)
 $Q = \text{Holding}$

Change G from 1 to 0.
 $Y = \text{holding the value of } D \text{ just before } G \text{ changed}$



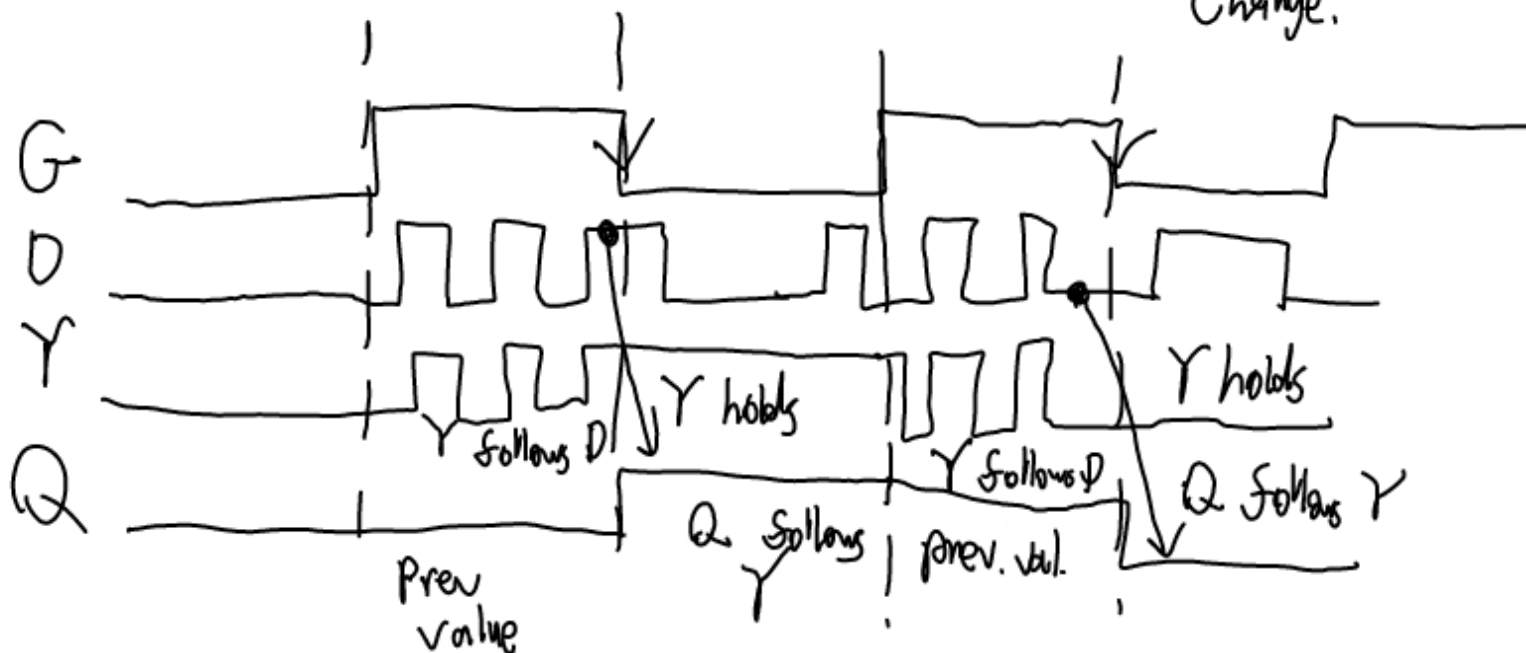
$Q = Y$ (Q follows Y)
 $= D \text{ just before change.}$



\Rightarrow Edge Sensitive

Negative-Edge Triggered flipflop

Symbol:

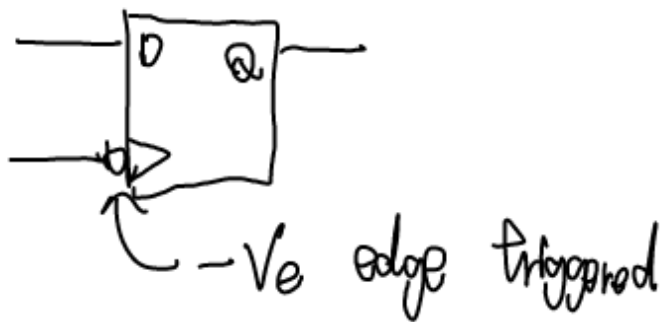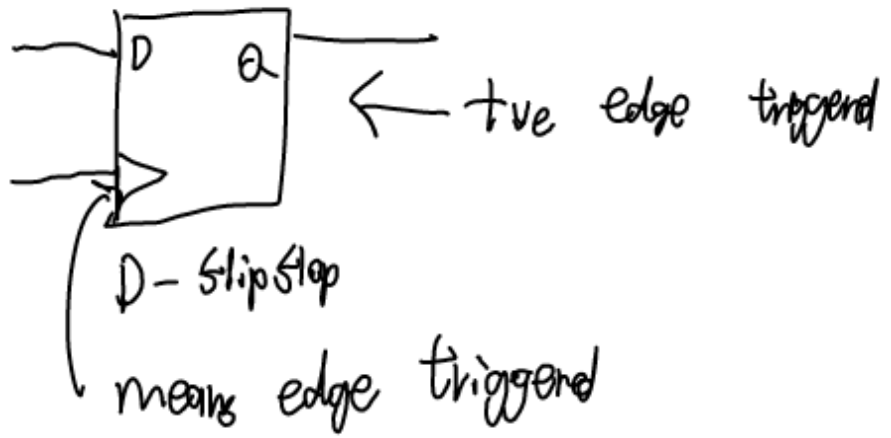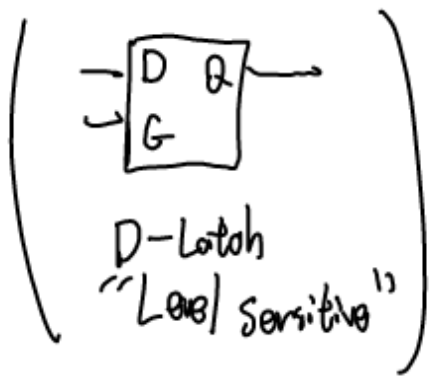

Gate

