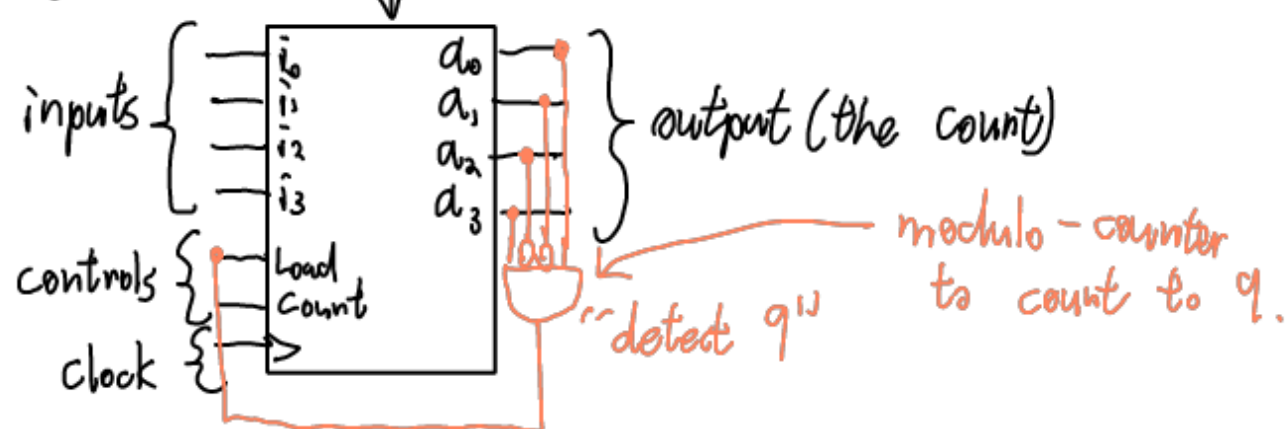


Last Time:

Binary Counters - both asynchronous & synchronous
- count up or down.
- sequence is $0 \dots 2^n - 1$

0000 \rightarrow 0001 \rightarrow ... \rightarrow 1111
 \uparrow

e.g., 4 bit binary up-counter



Modulo-Counter

Doesn't count all the way to $2^n - 1$.

e.g., modulo-10 counter counts 0...9


0000 \rightarrow 0001 \rightarrow ... \rightarrow 1001
 \uparrow

* Can you do this given a binary counter.

* Look at above diagram *

Clocked Sequential Circuits

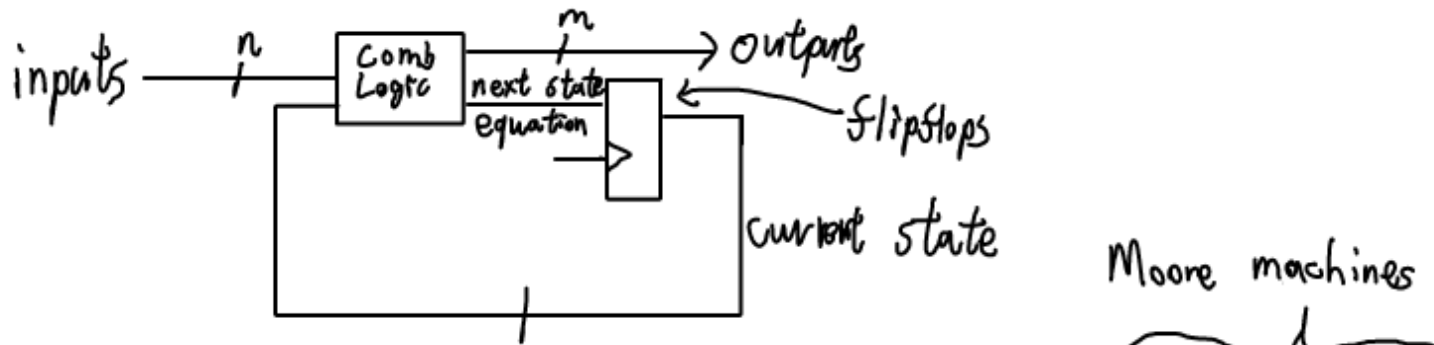* Counters / Registers are one example of a clocked sequential circuit.



Outputs can be either a function of the current state only or both the current state and the inputs.


Mealy machines

State Diagrams

* Sequential Circuits are represented abstractly via a state diagram.


- bubbles to represent states
- directed edges to represent transitions between states based on input.
- outputs labeled appropriately.

e.g.,

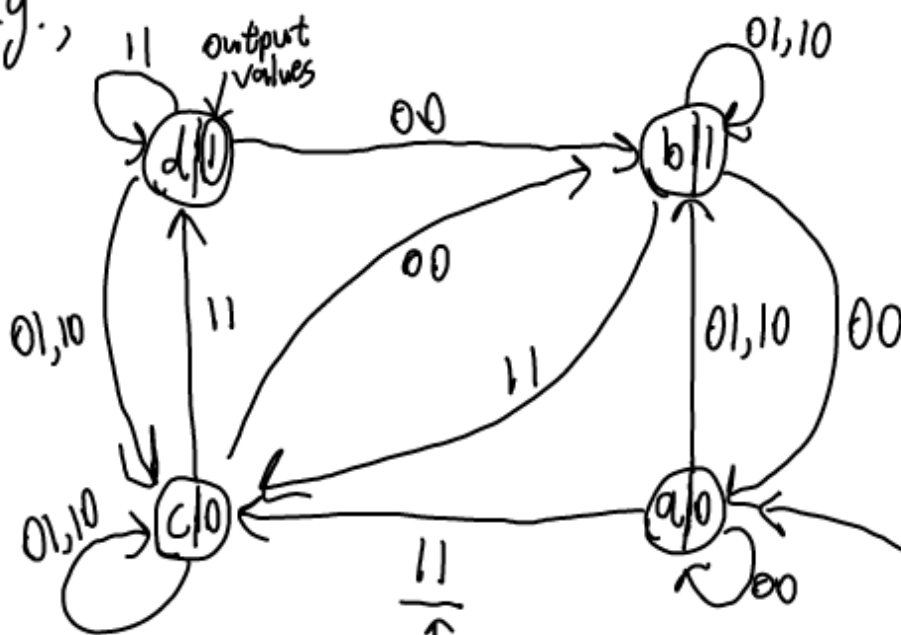

input values that cause me to go $a \rightarrow c$

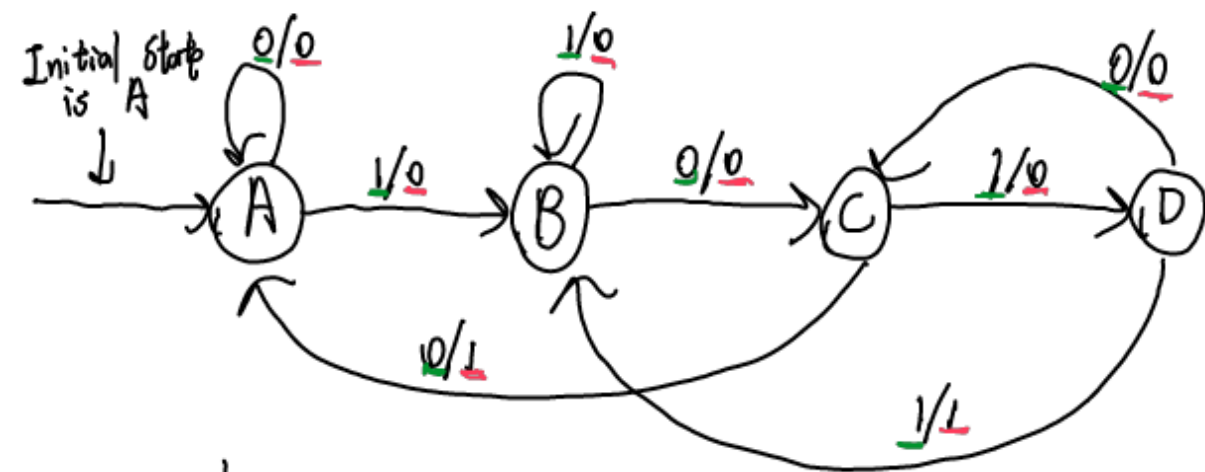⇒ 1 output
4 states: a, b, c, d
⇒ 2 inputs
Outputs inside bubbles
⇒ depend only on state
∴ Moore State Diagram



input / output

\Rightarrow 1 input

\Rightarrow 1 output

4 states

depends on state and input

\therefore Mealy Machine

X: 00110111101000-----
 state: A A B B C D B B B B C D C A A-----

Z: 000001000001000-----

\Rightarrow This circuit outputs 1 when it sees the 4 bit pattern "1101" at the input.

"sequence detector"