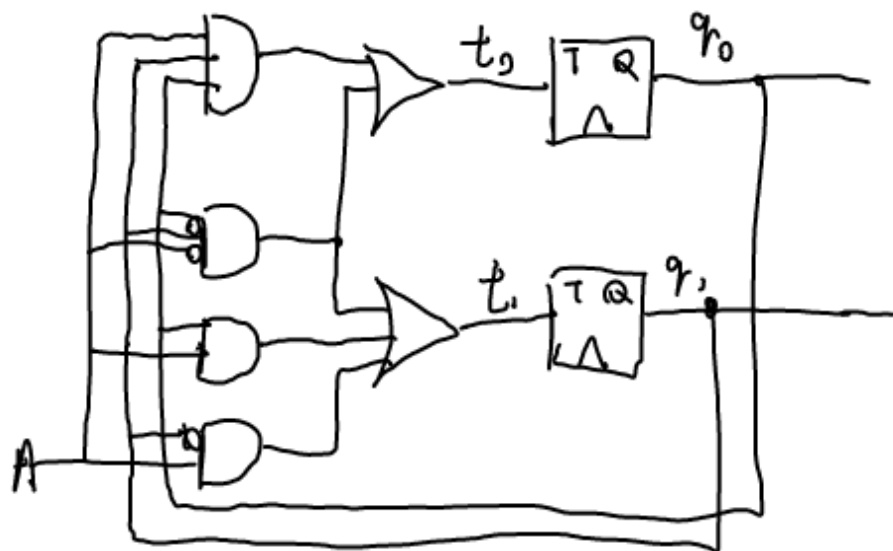


$q_1 q_0$	a	0	1
00	0	0	1
01	0	0	1
11	0	0	1
10	1	1	0

$q_1 q_0$	a	0	1
00	0	0	0
01	0	0	0
11	0	0	1
10	1	1	0

$$t_0 = a q_1 q_0 + \bar{a} q_1 \bar{q}_0$$

$$t_1 = a \bar{q}_1 + a q_0 + \bar{a} q_1 \bar{q}_0$$



JK:

$q_1 q_0$	a	0	1
00	0	0	1
01	0	0	1
11	X	X	X
10	X	X	X

$q_1 q_0$	a	0	1
00	X	X	X
01	X	X	X
11	0	1	1
10	1	0	0

$q_1 q_0$	a	0	1
00	0	0	0
01	X	X	X
11	X	X	X
10	1	0	0


$q_1 q_0$	a	0	1
00	X	X	X
01	0	0	0
11	0	1	1
10	X	X	X

State Assignment

* Typically, a state diagram has symbolic names for states \rightarrow We need to assign binary patterns to each state \rightarrow called state assignment.

* Different ways to do it.

Example:

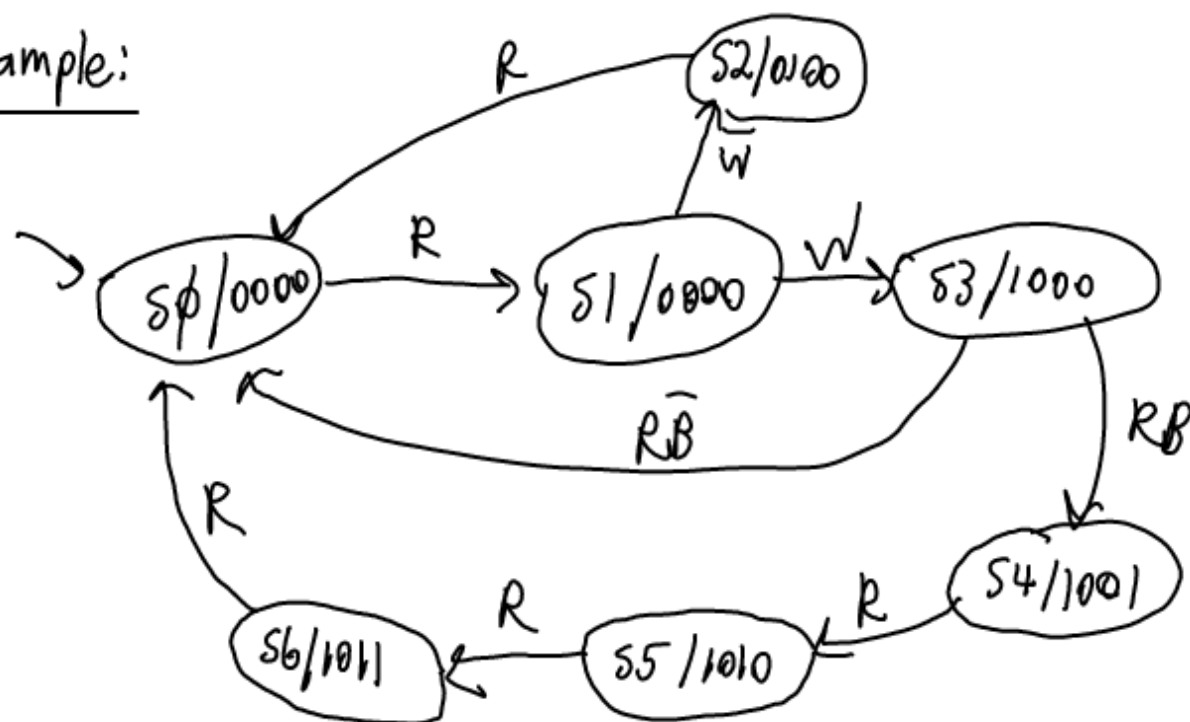

3 inputs / 4 outputs.

Method 1: Minimum number of flipflops.

* Use binary patterns s.t. we use as few FFs as possible.

n states $\rightarrow \lceil \log_2 n \rceil$ FFs

In this example, we need 3 FFs.

one pattern to one state. If all binary patterns are not used it's okay.

Here are unused states

S0	←	000
S1	←	001
S2	←	010
S3	←	011
S4	←	100
S5	←	101
S6	←	110
		111


etc

Method 2: Output Encoding

* Sometimes we can take circuit outputs directly from the state. (i.e., no output logic). (maybe appropriate for a moore machine).

State	Output	extra bit
S0	0000	0
S1	0000	1
S2	0100	0
S3	1000	0
S4	1001	0
S5	1010	0
S6	1011	0

In this example:

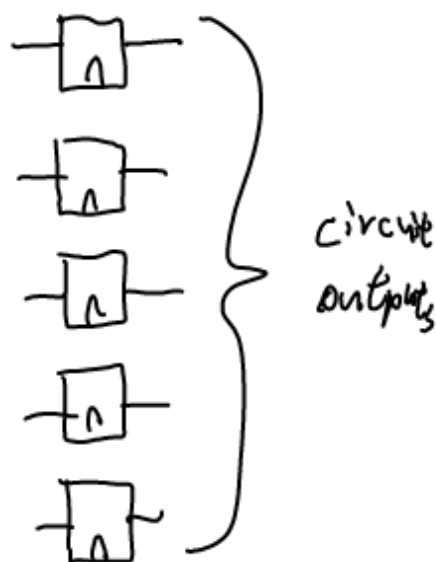

Method 3: One-hot encoding

* use one ff for each state
 n states $\rightarrow n$ ffs.

binary pattern for state j is

00 ... 010 ... 0
 \uparrow
 j

S0 \leftarrow 0000001
 S1 \leftarrow 0000010
 S2 \leftarrow 0000100
 S3 \leftarrow 0001000
 S4 \leftarrow 0010000
 S5 \leftarrow 0100000
 S6 \leftarrow 1000000

disadvantage: lots of FFs
 advantage: - logic usually simple
 (for input AND output)
 - if DFFs can go straight to circuit.

Example:

