
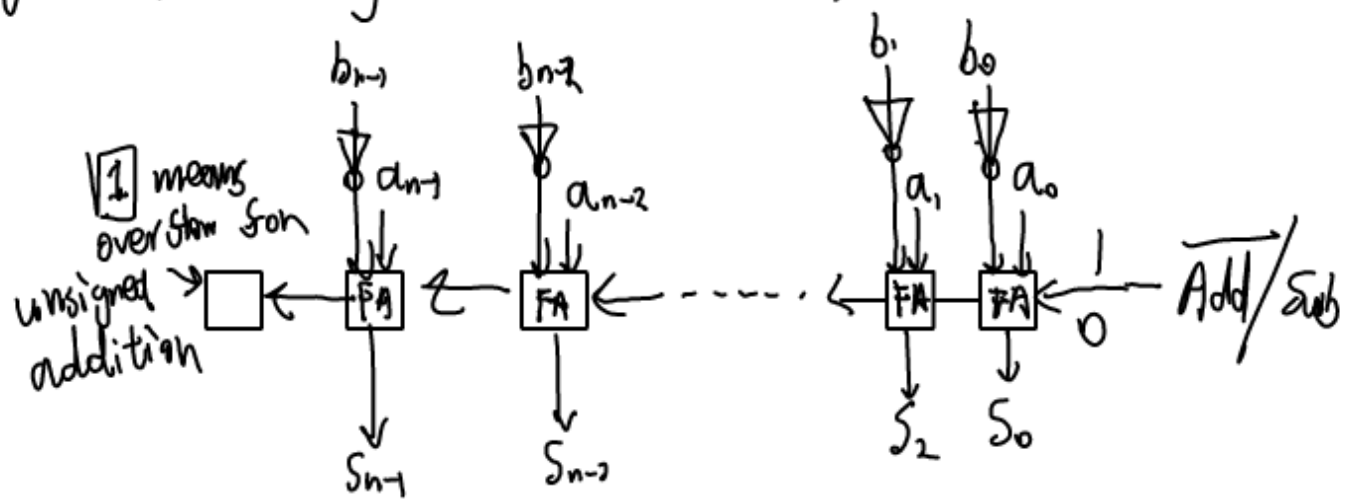


 
* Make a circuit that can both add & subtract unsigned #'s. Using stuff we already have.



0 means add
1 means sub.



if $f = x$ use XOR

 

Signed Integers

Q. how to represent signed ints?

0000 1001

+9 in 8-bits

-9?

1000 1001
-9

technique #1:

use sign bit + then other bits for magnitude.
(sign + magnitude)

We actually already have the correct solⁿ.

⇒ use 2's complement for -ve #'s.

00001001 → 11110111 ← the actual value is "encoded" inside all the bits.
 +9
 ↗
 Not really a sign bit anymore, but a leading "1" does mean the # is negative.

1101 ← What is this #?

→ unsigned? 1+0+4+8=13
 → signed?

→ sign + mag? -5

→ 2's complement? 1101 → 2's neg → 0011
 3

Overflow for signed #'s.


70
 +80
 150

01000110
 +01010000
 10010110




Doesn't indicate overflow for signed ints.

(-70)
 +(-80)
 -150

10111010
 +10110000
 10110110

 

MUX:

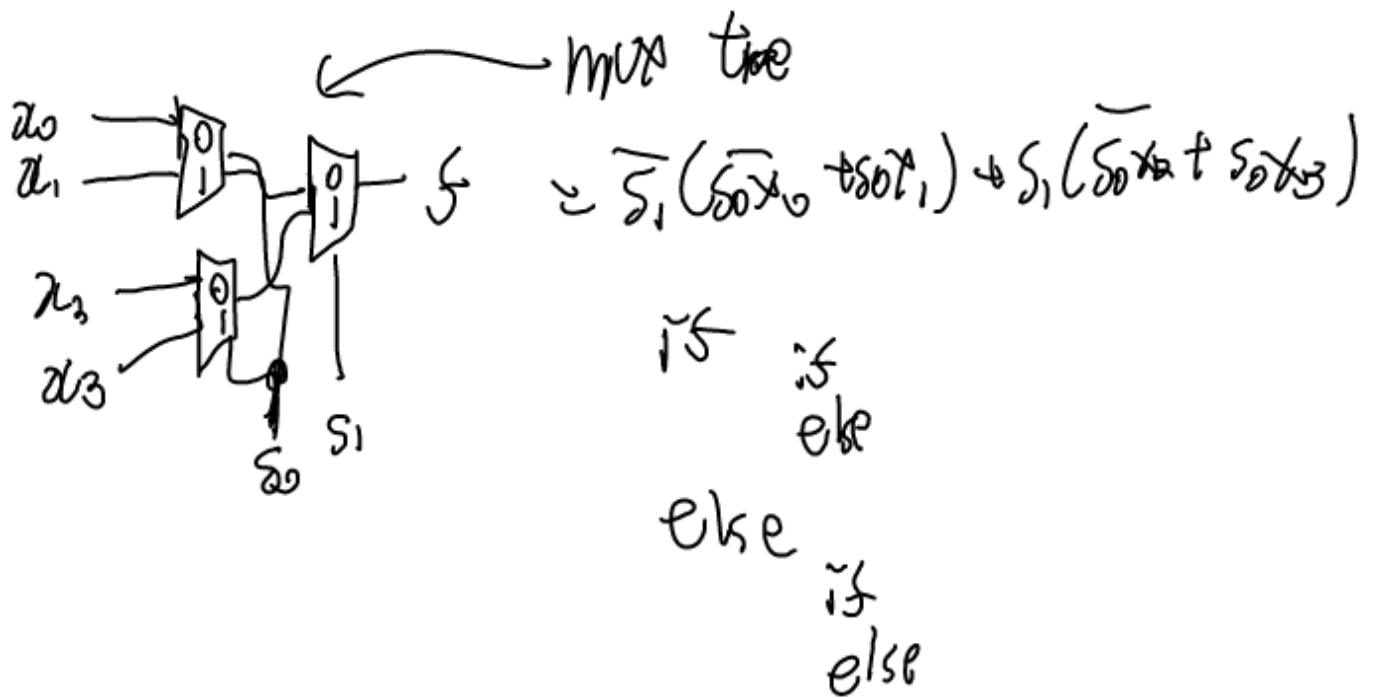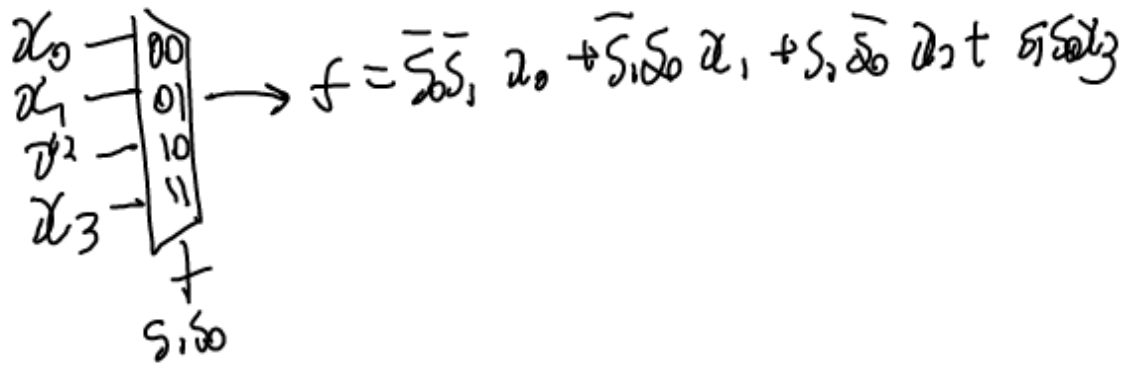 

MUX to impl. logic functions

* Any n -input function can be implemented with a MUX with $n-1$ select lines.

x_0	x_1	x_2	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

3 input & using minterms
 3 - select lines

