

We can also implement a function f using MUXES right from the Boolean Equation.


e.g., Implement f using only 2-input MUXES

$$f = abc + \bar{a}b + \boxed{\bar{b}\bar{c}} \quad \boxed{bc(a + \bar{a})}$$

$$= \bar{a}(b + \bar{b}\bar{c}) + a(bc + \bar{b}\bar{c})$$


$$= \bar{a}(\bar{c}(\bar{b} + b) + cb) + a(\bar{c}(\bar{b}) + c(b))$$

doesn't go all the way back

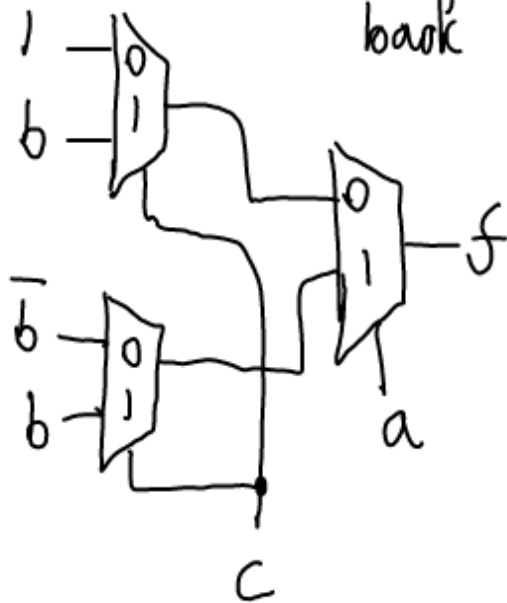

1

goes all the way back

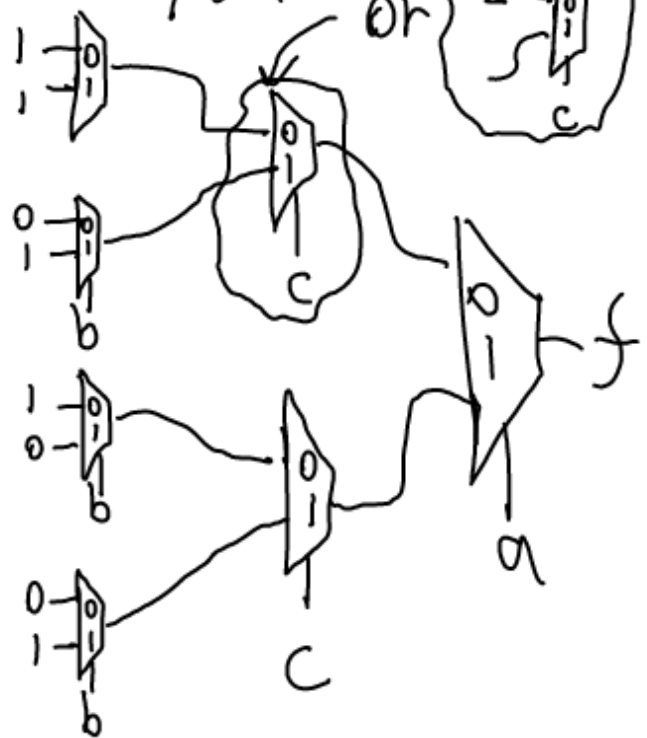


or



$$f = \bar{b}(\bar{c}) + b(\bar{a} + a\bar{c})$$
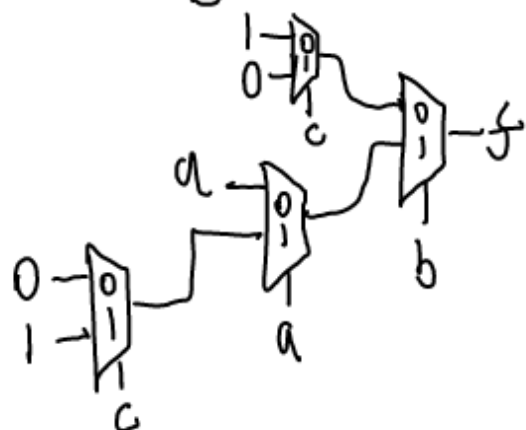
$$= \bar{b}(\bar{c}(1) + c(0)) + b(\bar{a}(1) + a(0))$$



$$+ b(\bar{a}(1) + a(\bar{c}(0) + c(1)))$$


Shannon Decomposition (BDD)

Decoders

→ $0 \dots 2^n - 1$

* We have a binary pattern in n -bits and we want to set one output to 1 based on the input value.


e.g.,

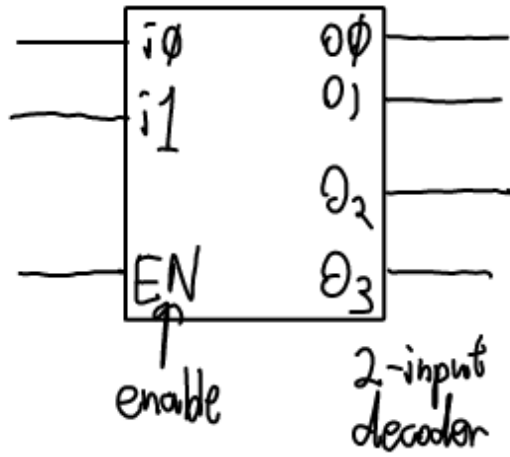

i_1	i_0	EN	o_0	o_1	o_2	o_3
x	x	0	0	0	0	0
0	0	1	1	0	0	0
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	1

$$o_0 = \overline{i_1} \overline{i_0} EN$$


$$o_2 = i_1 \overline{i_0} EN$$

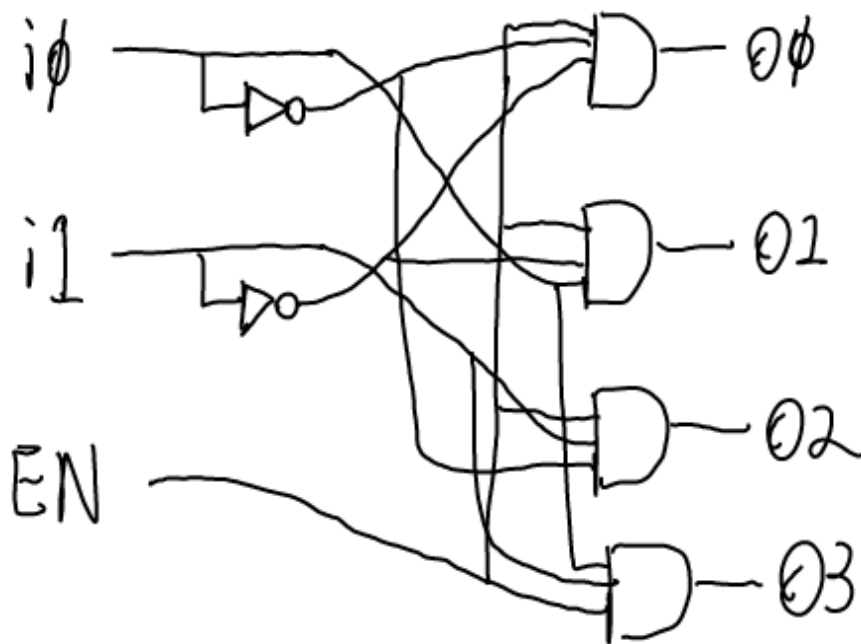

Decoder Trees


build a 4-to-16 decoder. Using 2-to-4 decoders.

i_3	i_2	i_1	i_0	
0	0	4		0-3
0	1	4		4-7
1	0	4		8-11
1	1	4		12-15

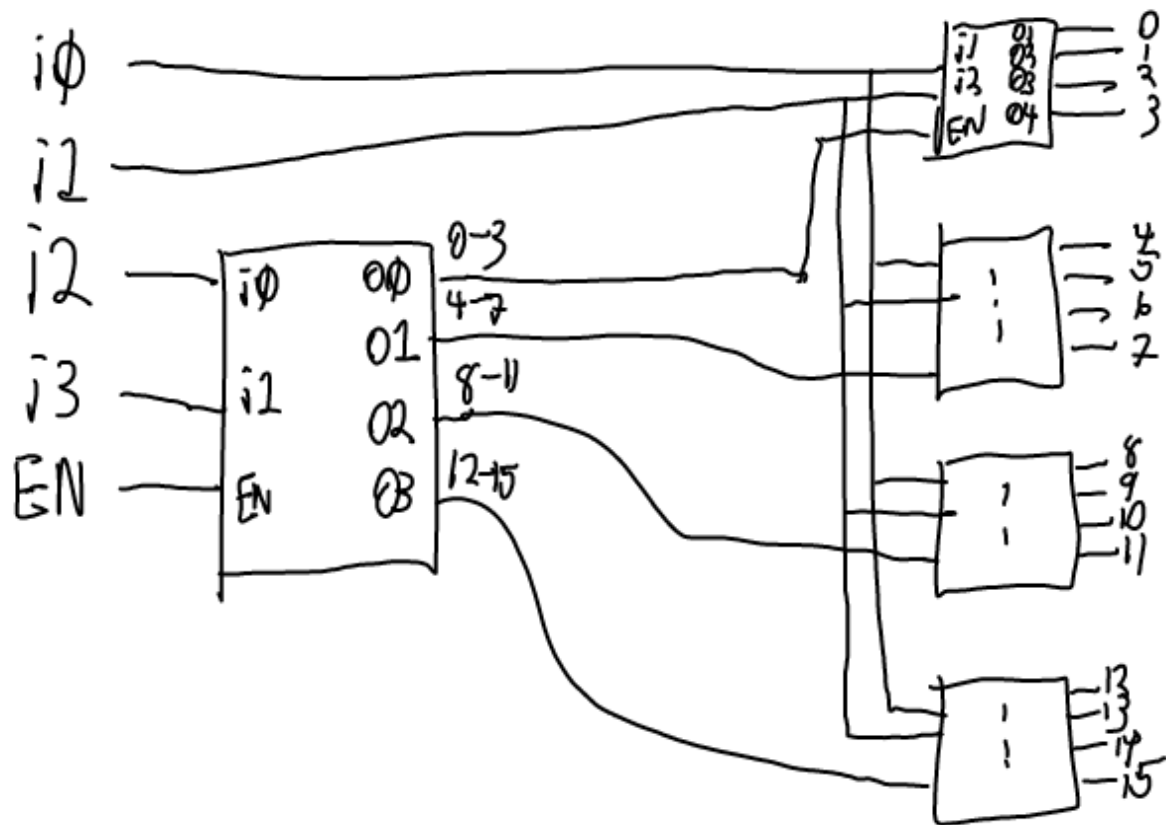

Make $f = abc + \bar{a}b + b\bar{c}$ using a decoder.

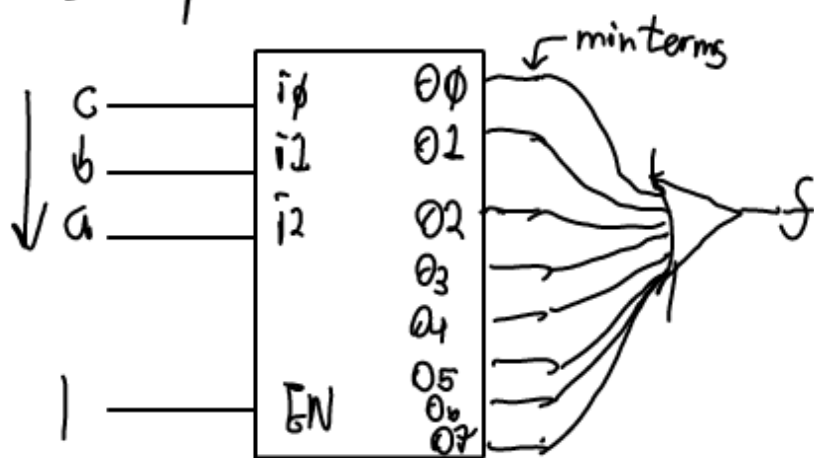$\Rightarrow 3$ inputs $\Rightarrow \therefore 3$ -to-8 decoder.



a	b	c	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Encoder

* opposite to decoder

* has 2^n input lines and n outputs

* output is the binary value of the input line which is 1.

i_3	i_2	i_1	i_0	01	00	valid	$00 = i_1 + i_3$	$01 = i_2 + i_3$
0	0	0	0	0	0			
0	0	1	0	0	1			
0	1	0	0	1	0			
0	1	1	0	1	1			
1	0	0	0	0	0			
1	0	1	0	0	1			
1	1	0	0	1	0			
1	1	1	0	1	1			

Problems

* What if multiple inputs are 1?

⇒ Ok... make it a priority encoder

(highest #ed input is the one that matters)

(derive equation for final exam)

* What if all zeroes?

make another output to check for error.

i_3	i_2	i_1	i_0	valid
0	0	0	0	0