

Today

State Tables

* Shows same info as state diagram but in different form,

Curr. State	next state		output (z)	
	x=0	x=1	x=0	x=1
a	a	b	0	0
b	c	b	0	0
c	a	d	0	0
d	c	b	0	1

Sequential Circuit Design

* Procedure to implement a state diagram/table in/as a digit circuit.

Steps: 1) Given a verbal description, decide on states, draw diagram/table

2) Try to reduce the number of states (state reduction)

3) If states are "english names", then assign binary numbers to each state \Rightarrow diagram/table now only has "1"s + "0"s. (state assignment)



4) Pick a FF type (DFF, TFF, JK FF) to hold the state. The # of FFs depends on how many bits are needed.

5) Derive FF input eqns. (next state eqns)

  6) Derive output eqns. 7) Draw Circuit.

Eg. Design a controller for a vending machine that accepts nickels (n) and dimes (d) and opens a door once 15¢ is deposited.


Define the states as "amount deposited so far."



* State Assignment

$=0¢ \rightarrow 0 \rightarrow 00$	state appear in circuit or FF outputs
$=5¢ \rightarrow 1 \rightarrow 01$	
$=10¢ \rightarrow 2 \rightarrow 10$	
$\geq 15¢ \rightarrow 3 \rightarrow 11$	

 
* FF selection \Rightarrow Need 2 of them; pick DFFs.



State table in terms of binary values

	Curr. state		next state (q_1, q_0)				output (open)				ss input (d_1, d_0)			
			nd				nd				nd			
	q_1, q_0		00	01	10	11	00	01	10	11	00	01	10	11
0 ϕ	0 0		00	10	01	XX	0	0	0	X	00	10	01	XX
5 ϕ	0 1		01	11	10	XX	0	0	0	X	01	11	10	XX
10 ϕ	1 0		10	11	11	XX	0	0	0	X	10	11	11	XX
15 ϕ	1 1		11	00	00	XX	1	1	1	X	00	00	00	XX

 * ss input values (d_1, d_0) depend on FF type AND next state *



* Input Eqs. (next state eqns)

q_1, q_0	d_0					d_1			
	00	01	11	10		00	01	11	10
00	0	0	X	1		0	0	X	1
01	1	1	X	0		0	0	X	0
11	0	0	X	0		0	0	X	0
10	0	1	X	1		0	0	X	0